



# COLLEGE OF ENGINEERING & TECHNOLOGY

Department : Electrical and Control Engineering

Lecturer : Dr. Mostafa Saad

Course : Power System II

Course Code : EE441

Date : 21 /1/2015

Marks : 40

Time : 2 hour

## Final Exam

Answer the following questions:-

### Question 1 : (B2)

The network shown in Fig.1 shows single line diagram of a single power network, the bus impedance matrix is given below. Each generator connected to buses 1 and 4 has a sub-transient reactance of 0.25 pu, all line impedances are in pu. Making the usual fault study assumptions;

- Determine the sub-transient current in pu for a three-phase fault on bus 3
- Determine the contributions to the fault current from 1 to 3 and from 4 to 3.

$$Z_{bus} = \begin{bmatrix} j0.135 & j0.123 & j0.128 & j0.114 \\ j0.123 & j0.146 & j0.124 & j0.126 \\ j0.128 & j0.124 & j0.149 & j0.122 \\ j0.114 & j0.126 & j0.122 & j0.135 \end{bmatrix}$$

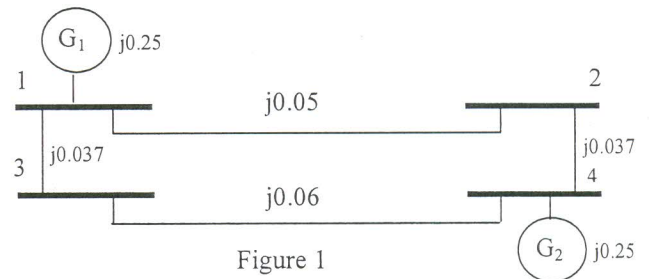


Figure 1

(7 marks)

### Question 2: (B2)

- Explain in details the symmetrical component method (3 marks)
- A three-phase line feeding a balanced-Y load has one of its phases (phase b) open. The load neutral is grounded, and the unbalanced line currents are

$$I_p = \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 10/0^\circ \\ 0 \\ 10/120^\circ \end{bmatrix} \text{ A}$$

- Draw the circuit
- Calculate the sequence currents
- Calculate the neutral current.

(4 marks)

### Question 3 :

- For a three-phase system, a single line-to-ground fault occurs through a fault impedance  $Z_F$ , deduce the fault conditions in phase domain and sequence domain and draw the interconnected sequence networks. (A18)(4 marks)
- A single-line diagram of a power system is shown in Figure 2. The negative- and zero-sequence reactances are also given. The neutrals of the generator and  $\Delta$ -Y transformers are solidly grounded. The motor neutral is grounded through a reactance  $X_n = 0.05$  pu on the motor base.
  - Draw the per-unit zero-, positive-, and negativesequence networks on a 100-MVA, 13.8-kV base in the zone of the generator.
  - Reduce the sequence networks to their Thevenin equivalents, as viewed from bus 2. Prefault voltage is  $V_F = 1.05 \angle 0^\circ$  pu. Prefault load current and  $\Delta$ -Y transformer phase shift are neglected.

Members of course Examination Committee:		Signature:	Date:
Lecturer:	Dr. Mostafa Saad		3/1/2015
Course Coordinator :	Prof. Amany Ahmed		3/1/2015
Head of Department:	Prof. Hamdy Ashour		3/1/2015

