



Lecture 2
EC560 - Modern Electronics Circuits
Performance Evaluation
S-Parameters, Passive Elements in RF
Amr Bayoumi



Outline

Transceiver Performance Evaluation

- **Signal-to-Noise Ratio (SNR)**
- **Noise Figure (NF)**
- **Sensitivity**
- **Reflection:**
 - S-Parameters
- **RF models of passive components**



Signal-to-Noise Ratio (SNR)

- Indication of signal strength

$$\text{SNR}_{\text{Ratio}} = \text{Signal Power} / \text{Noise Power}$$

$$= P_{\text{Signal}} / P_{\text{Noise}} = (A_{\text{signal}} / A_{\text{Noise}})^2$$

$$\text{SNR}_{\text{dB}} = 10 \log (\text{SNR ratio}) = 10 \log (P_{\text{Signal}} / P_{\text{Noise}})$$

$$= 20 \log (A_{\text{signal}} / A_{\text{Noise}})$$




Noise Figure (NF)

- Measure of SNR degradation by the circuit block, due to internally generated noise

$$\text{Noise Figure (NF}_{dB}) = \text{SNR}_{in(dB)} - \text{SNR}_{out(dB)} \quad \text{all in dB}$$

$$\text{Noise Factor (F)} = \text{SNR}_{in} / \text{SNR}_{out} \quad \text{all in ratios (not dB)}$$

$$\text{NF} = 10 \log (F)$$

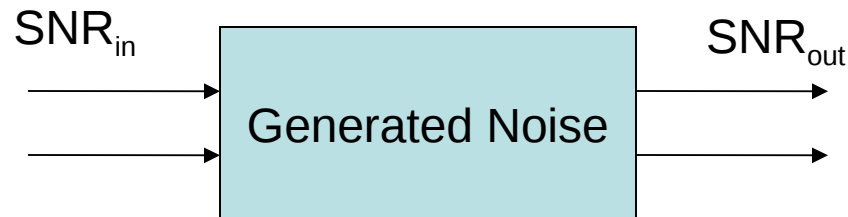



Sensitivity (in dBm)

- **Measurement Unit: dBm**
1dBm = 1dBmWatt = Power referenced to 1mW
= $10 \log (\text{Signal Power} / 1 \text{ mWatt})$
Zero dBm = 1mW, 10dBm = 10mW, 1dBm change = 2x change
- **Sensitivity = Minimum Detectable Signal Power (P_{\min})**
referenced to 1mW Signal
$$e = 10 \log (P_{\min} / 1\text{mW})$$
- The smaller the better, usually $P_{\min} < 1\text{mW}$, therefore e is negative (-60dBm, ...)
- -98dBm is better than -95dBm, and it detects half the power of -95dBm




S-Parameters Matrix

$$b_1 = S_{11} a_1 + S_{12} a_2$$

$$b_2 = S_{21} a_1 + S_{22} a_2$$

S-parameters are complex values

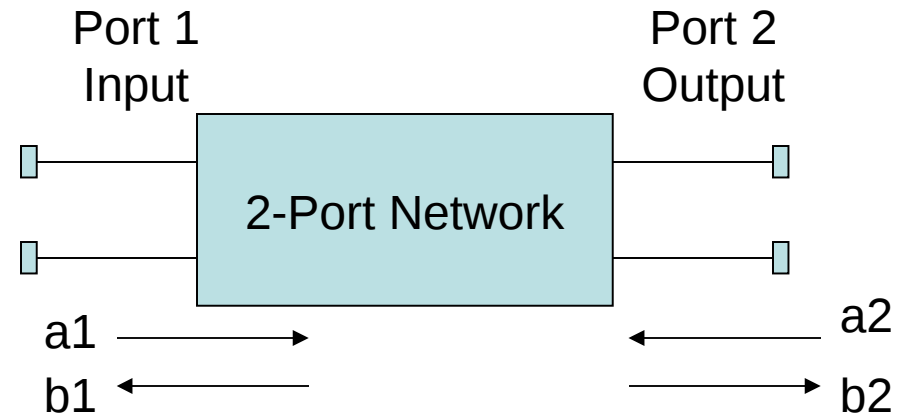

a_1 = Incident wave voltage at Port 1

a_2 = Incident wave voltage at Port 2

b_1 = Exiting wave voltage at Port 1

b_2 = Exiting wave voltage at Port 2

S_{11} = Input port voltage reflection coefficient


S_{12} = Reverse voltage gain

S_{21} = Forward voltage gain

S_{22} = Output port voltage reflection coefficient



Reflection Coefficient

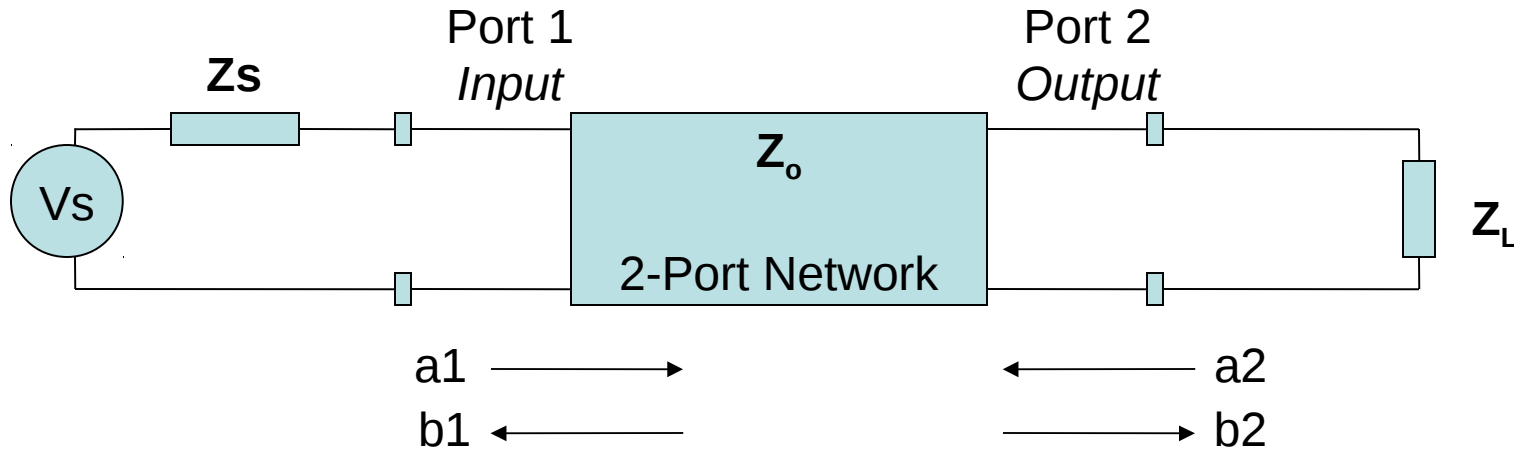


- Reflection Coefficient " Γ_1 " = b_1/a_1
= $Z_L - Z_0 / Z_L + Z_0$

@ $Z_L = Z_0 \Rightarrow \Gamma = 0$; @ $Z_L = 0 \Rightarrow \Gamma = -1$; @ $Z_L = \text{open} \Rightarrow \Gamma = 1$



S-Parameters: Max power Transfer

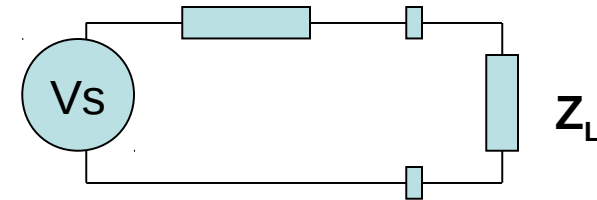- Antennas are example application
- Maximum power transfer to load at:
 $Z_L = \text{complex conjugate of } Z_s$



$$P = I_{rms}^2 R_L = 0.5 * \{V_{max} / (Z_s + Z_L)\}^2 R_L$$
$$= 0.5 * V_{max}^2 R_L / (R_s + X_s + R_L + X_L)^2$$

X_s, X_L are reactance (complex part of impedance)

Minimize: $(R_s + X_s + R_L + X_L)^2 = (R_s + R_L)^2 + (X_s + X_L)^2$



P_L is max at $X_L = -X_s \Rightarrow P = 0.5 * V_{max}^2 R_L / (R_s + R_L)^2$

By taking 1st & 2nd deriv. w.r.t. R_L , P_{max} @ $R_L = R_s$

Z_L @ Max power transfer to load = $R_s - X_s$





Capacitor RLC

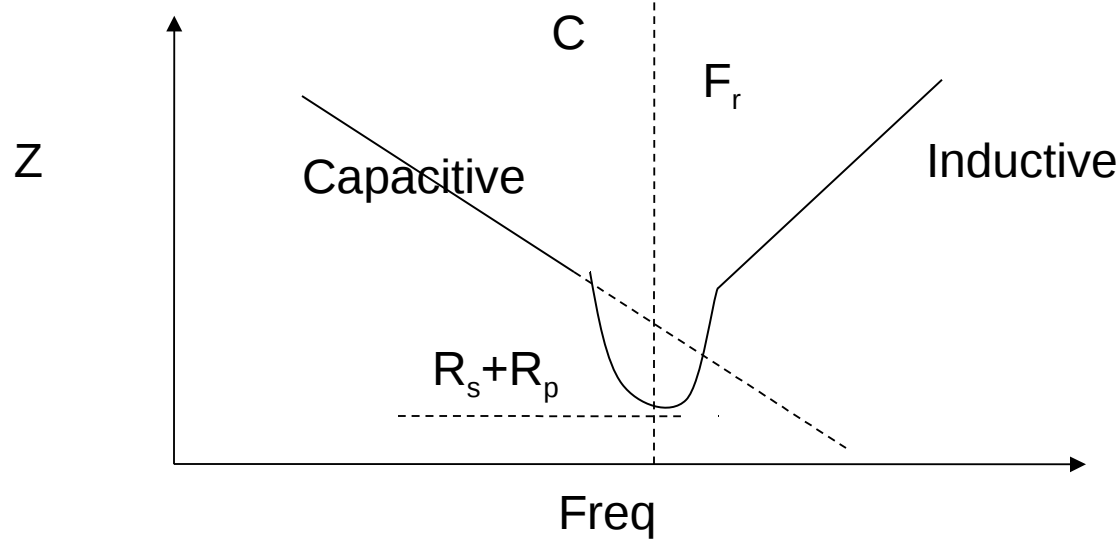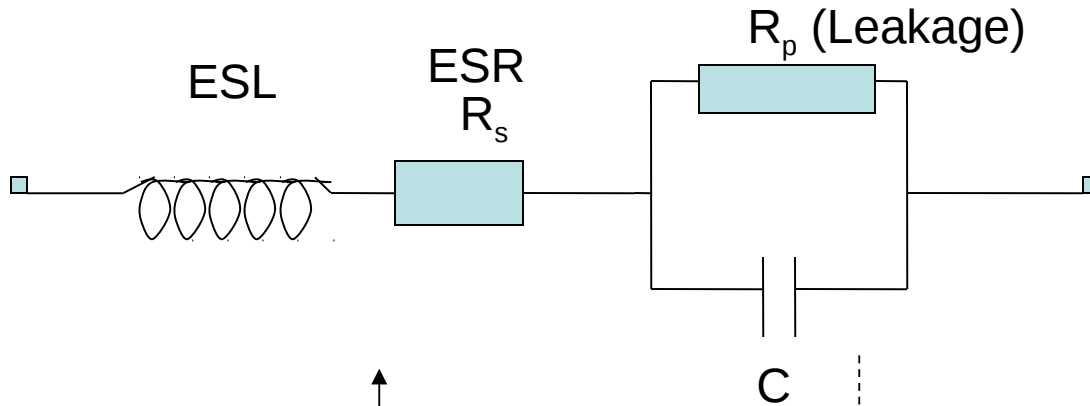





Coil RLC

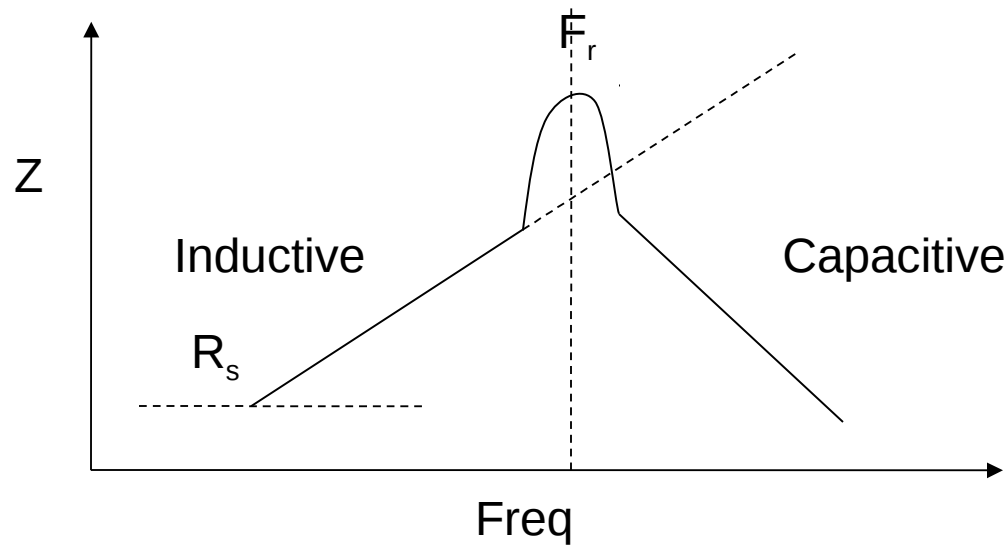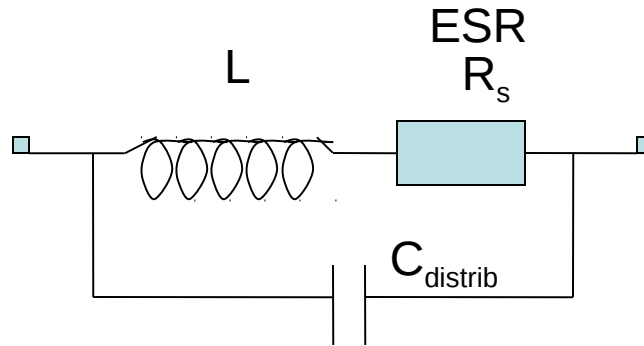



Resistor RLC

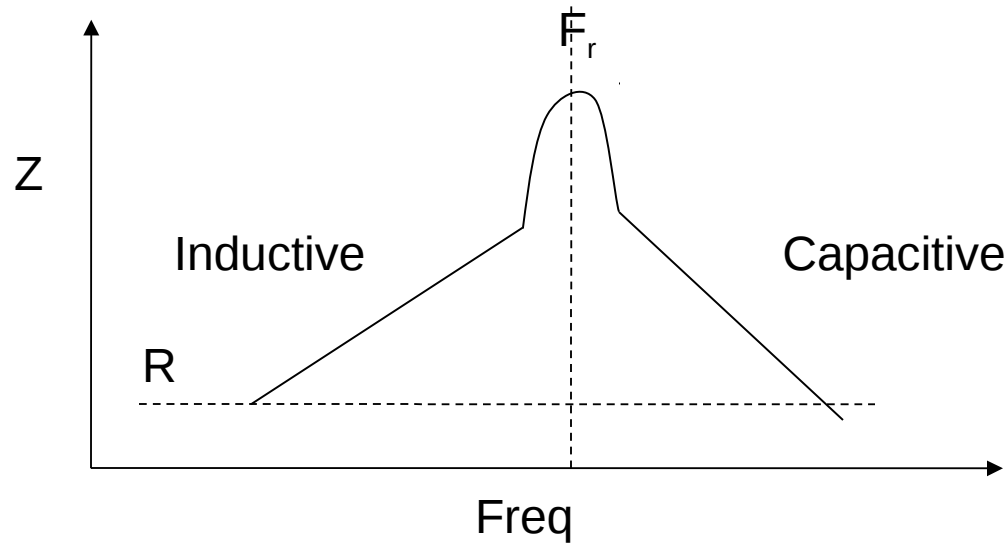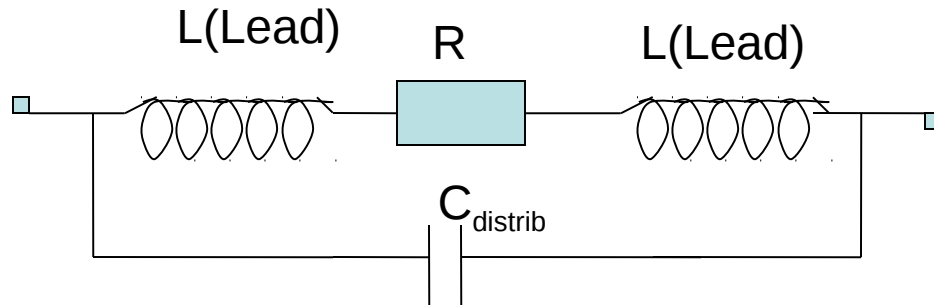



MOSFET Parasitics

- RLC for interconnects, not just C or R
- S/D substrate coupling
- Resistance of gate, channel Source/Drain
- S/D junction capacitance to gate, to substrate
- Substrate resistance to body contact
- MOSFET has input R&C, i.e. complex impedance => needs matching at RF!