

for figure a, b, c & d
find the closed loop gain.

$$\frac{V_o}{V_{in}}$$

Q2) Design Inverting Amplifier


Closed loop gain = -100.

a) Find R_1 & R_2

b) What is the max V_{in}

if $V_{sat} = \pm 10V$


Q3

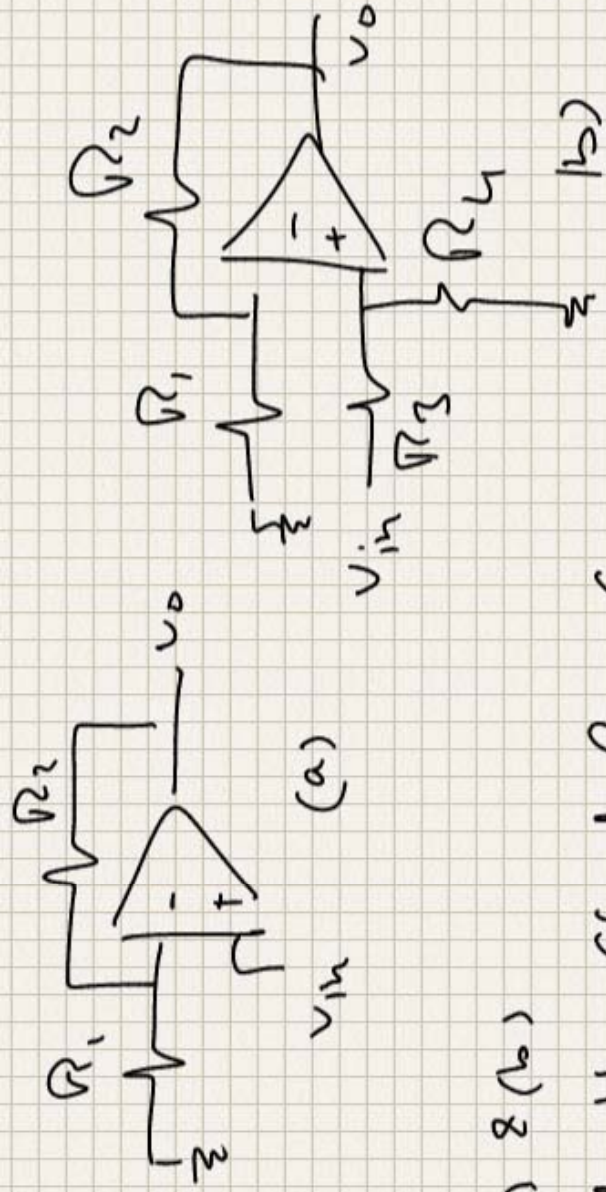


for (a) & (b)

find the closed loop gain.

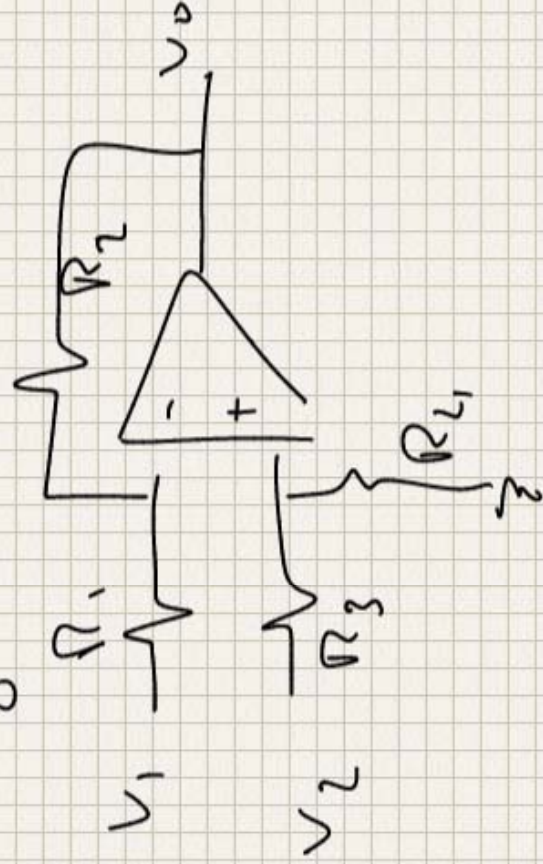Q4) for this figure find v_o $f(v_1, v_2)$ using superposition



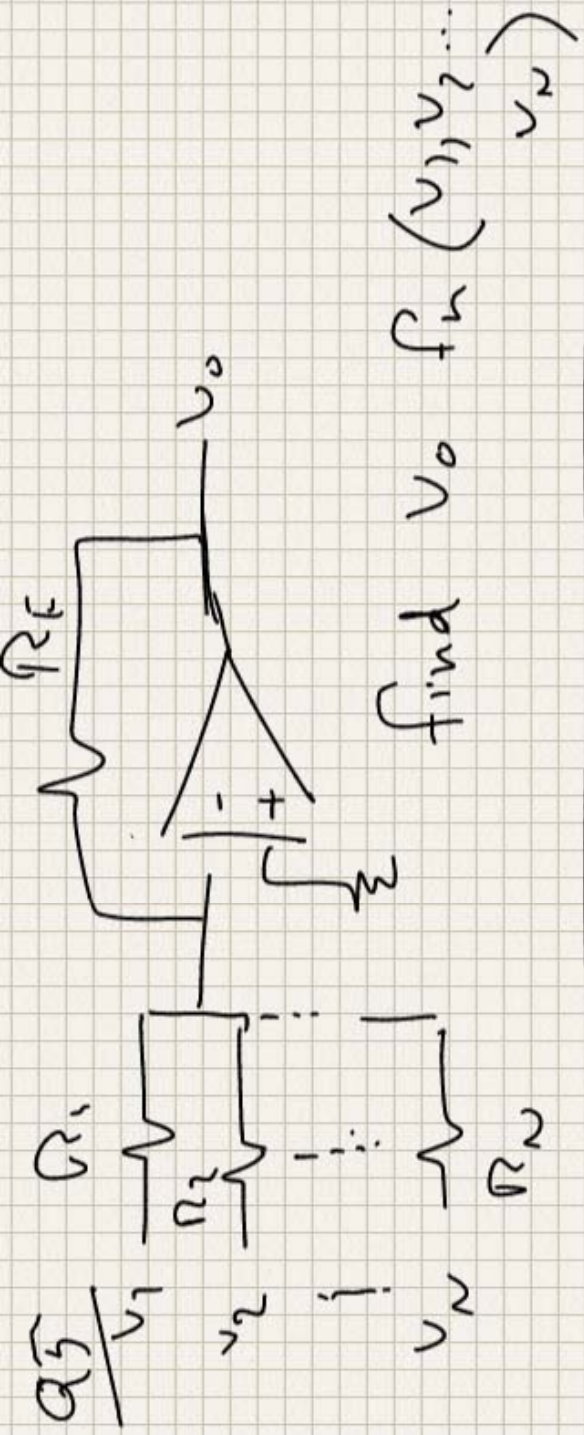b) if $R_1 = R_3$ $R_2 = R_4$ find $\left(\frac{v_o}{v_2 - v_1}\right)$



Q6 Design Using any number of op Amps & Resistors R

$$v_o = -(v_1 + 2v_2) + v_3$$

Q7

Design an amplifier

With Gain 11 Using op amp
