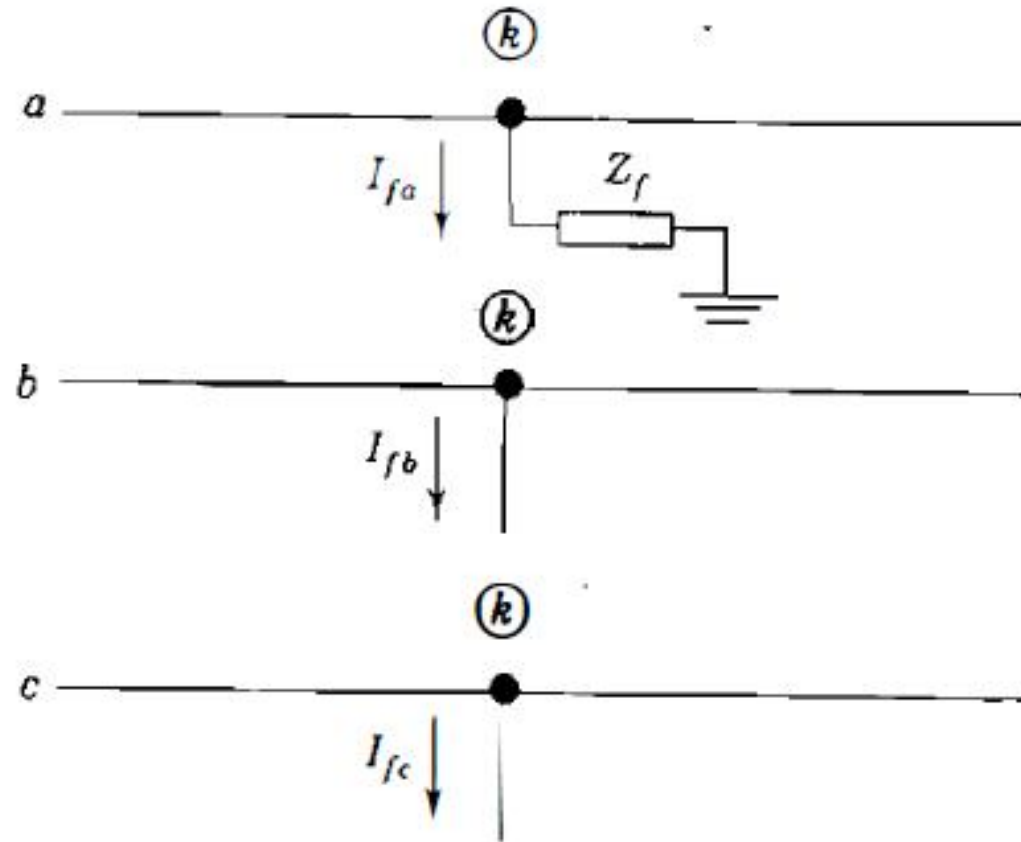


# Single Line to Ground Fault

---



$$I_{fb} = 0$$

$$I_{fc} = 0$$

$$V_{ka} = Z_f I_{fa}$$

$$\begin{bmatrix} I_{fa}^{(0)} \\ I_{fa}^{(1)} \\ I_{fa}^{(2)} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix} \begin{bmatrix} I_{fa} \\ 0 \\ 0 \end{bmatrix}$$

$$I_{fa}^{(0)} = I_{fa}^{(1)} = I_{fa}^{(2)} = \frac{I_{fa}}{3}$$

$$V_{ka}^{(0)} = -Z_{kk}^{(0)} I_{fa}^{(0)}$$

$$V_{ka}^{(1)} = V_f - Z_{kk}^{(1)} I_{fa}^{(0)}$$


$$V_{ka}^{(2)} = -Z_{kk}^{(2)} I_{fa}^{(0)}$$

Summing these equations and noting that  $V_{ka} = 3Z_f I_{fa}^{(0)}$  give

$$V_{ka} = V_{ka}^{(0)} + V_{ka}^{(1)} + V_{ka}^{(2)} = V_f - (Z_{kk}^{(0)} + Z_{kk}^{(1)} + Z_{kk}^{(2)}) I_{fa}^{(0)} = 3Z_f I_{fa}^{(0)}$$


Solving for  $I_{fa}^{(0)}$
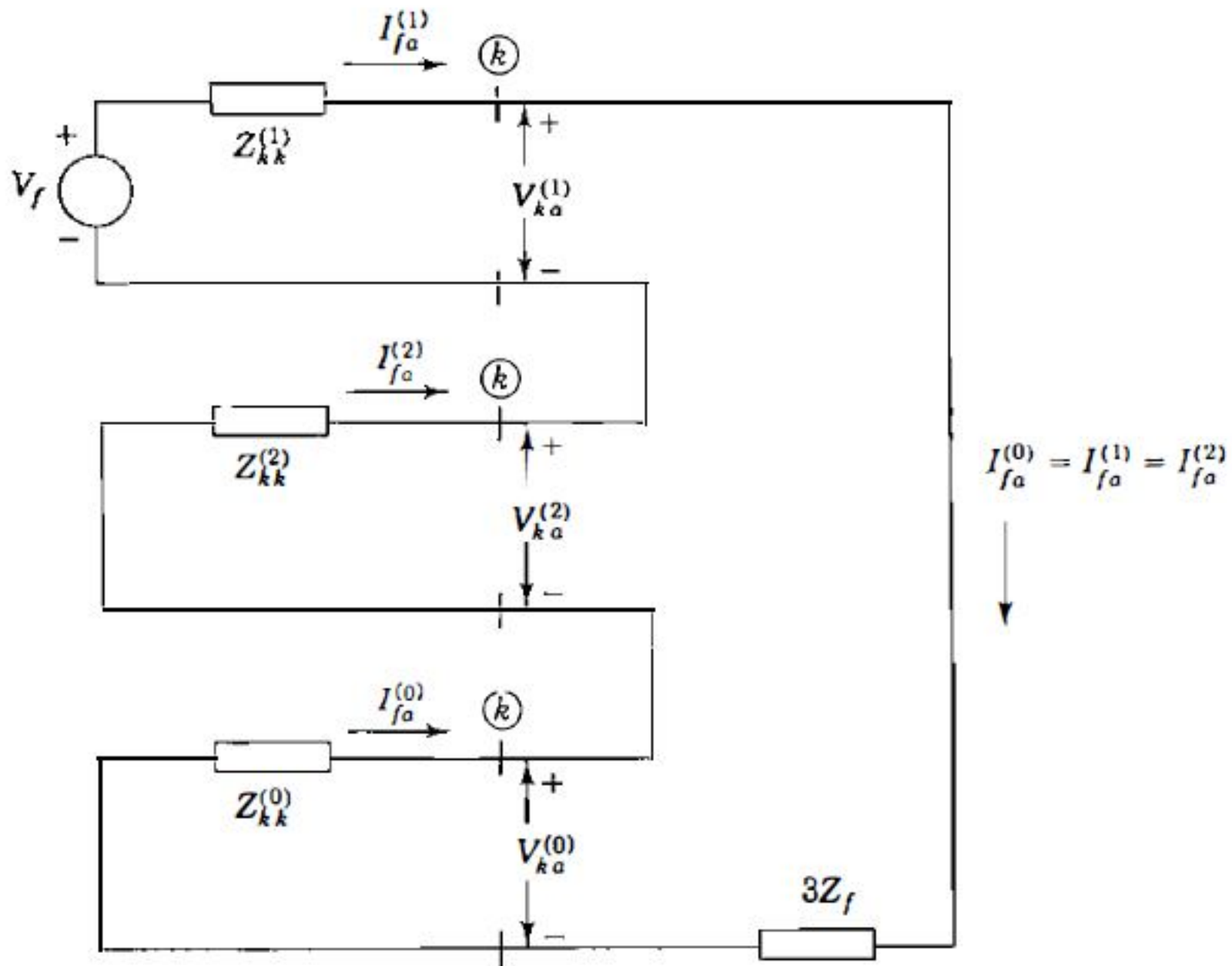
$$I_{fa}^{(0)} = I_{fa}^{(1)} = I_{fa}^{(2)} = \frac{V_f}{Z_{kk}^{(1)} + Z_{kk}^{(2)} + Z_{kk}^{(0)} + 3Z_f}$$



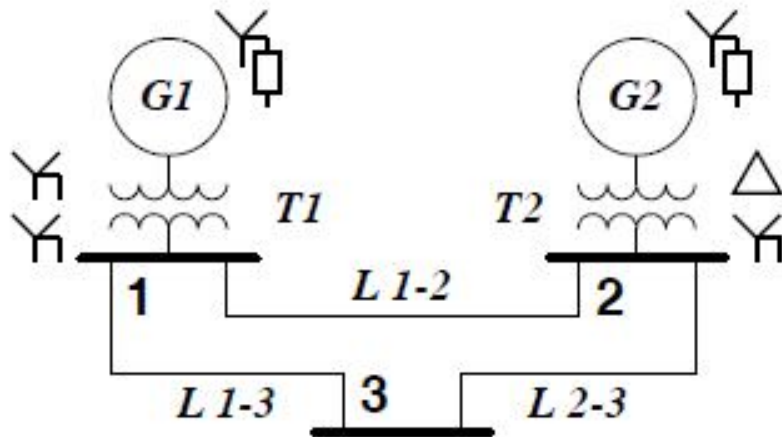
# Example

- ◆ The neutral of each generator is grounded through a current limiting resistor of 8.333 % on a 100 MVA base
- ◆ generators are running at no-load at rated voltage and in phase
- ◆ all network data is expressed on a 100 MVA base
- ◆ Find the fault current for 3-phs, 1-phs, At Bus Bar 3




<u>Item</u>	<u>V Rating</u>	<u>X1</u>	<u>X2</u>	<u>X0</u>
G1	20 kV	15%	15%	5%
G2	20 kV	15%	15%	5%
T1	20/200 kV	10%	10%	10%
T2	20/200 kV	10%	10%	10%
L 1-2	200 kV	12.5%	12.5%	30%
L 1-3	200 kV	15%	15%	35%
L 2-3	200 kV	25%	25%	71.25%

- **Positive Sequence Network**

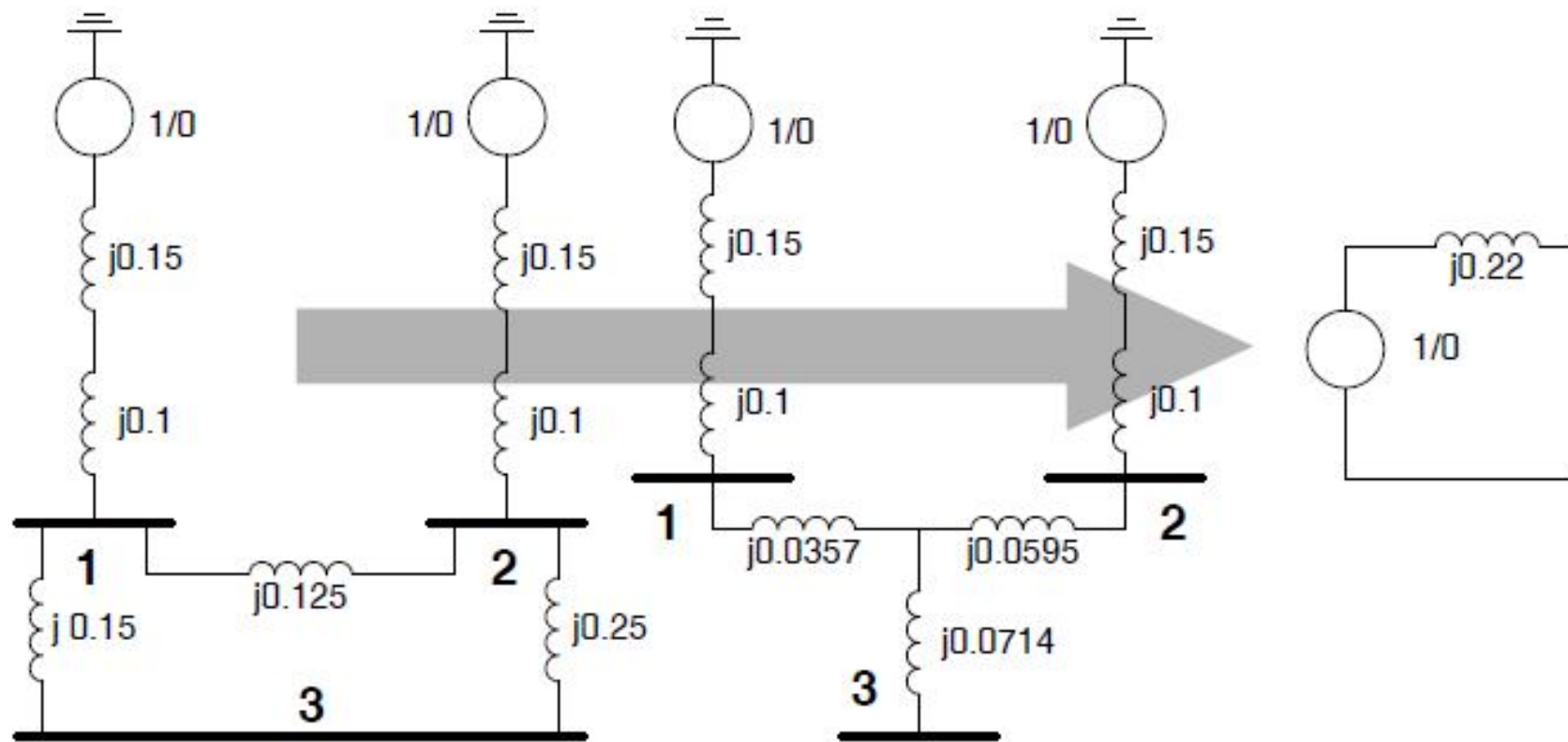


- **Negative Sequence Network**

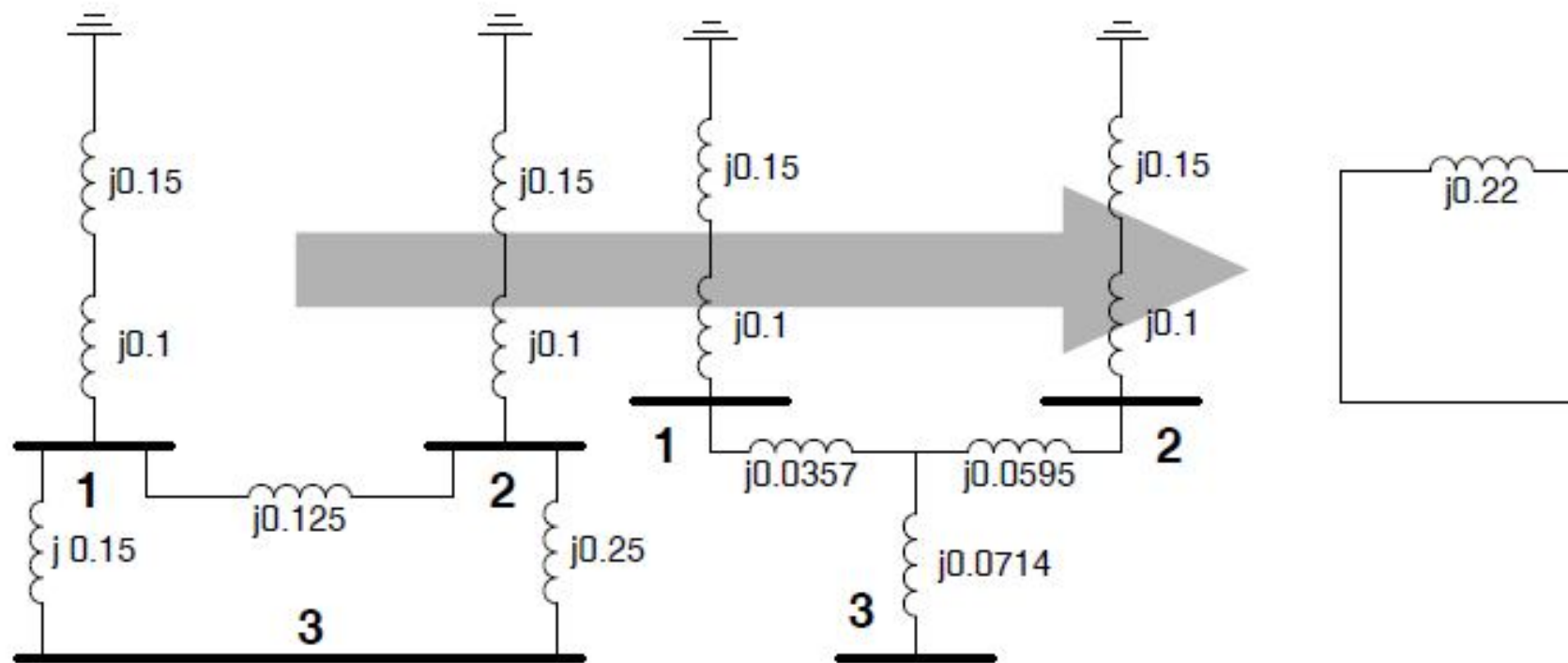



- **Zero Sequence Network**

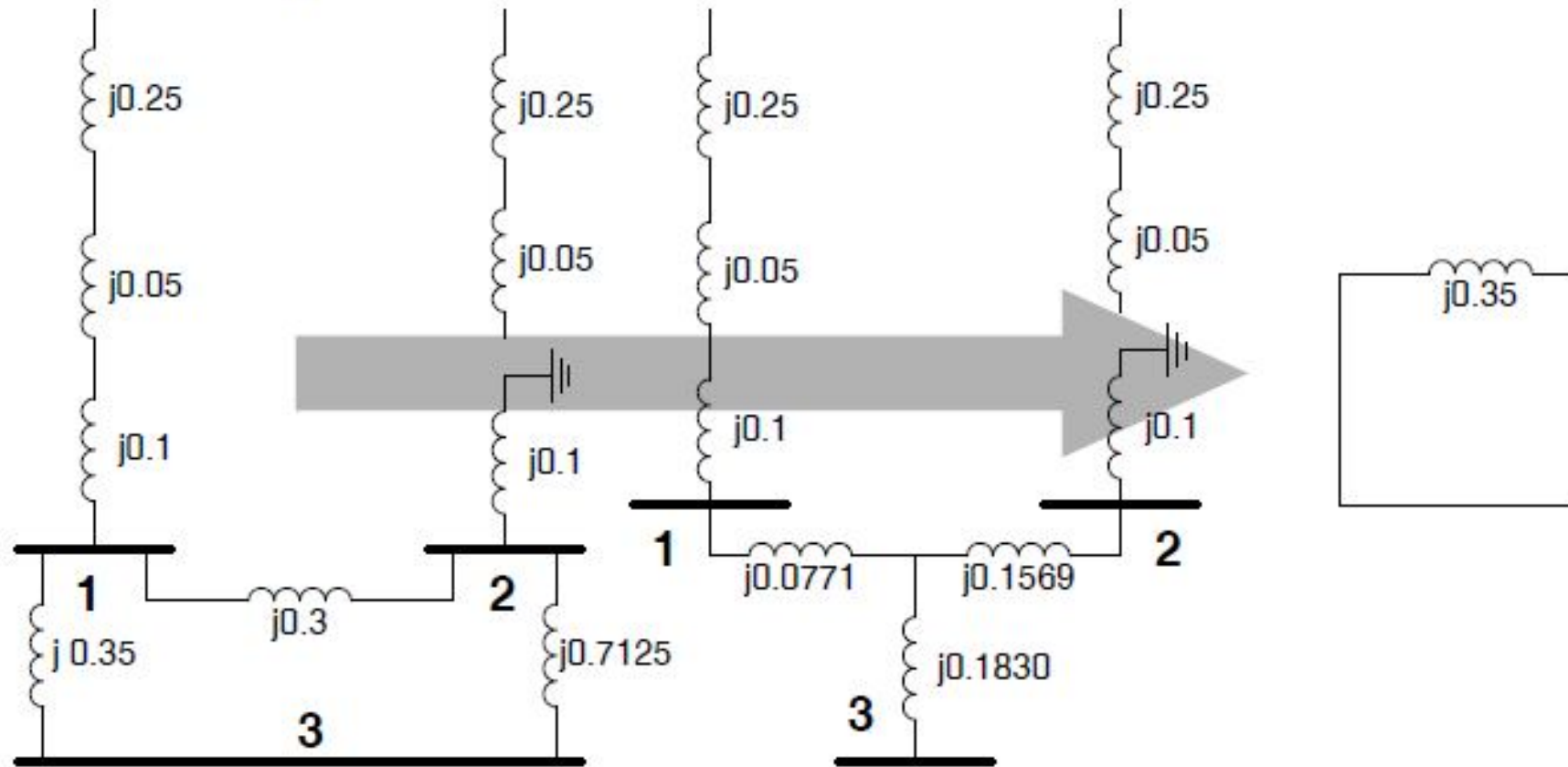

- **3-phase fault**

$$I_3^{a1}(F) = \frac{V_3^{a1}}{Z_{33}^1} = \frac{1.0 \angle 0^\circ}{j0.22} = -j4.54 \text{ pu}$$

$$I_{af} = I_3^{a1}(F) = -j4.54 \text{ pu}$$

- **SLG fault**

$$\begin{aligned} I_3^{a0} = I_3^{a1} = I_3^{a2} &= \frac{V_3^{a1}}{Z_{33}^0 + Z_{33}^1 + Z_{33}^2} \\ &= \frac{1.0 \angle 0^\circ}{j0.35 + j0.22 + j0.22} = -j1.266 \text{ pu} \end{aligned}$$

$$I_{af} = 3I_3^{a1} = -j3.80 \text{ pu}$$

**Example 12.1.** Two synchronous machines are connected through three-phase transformers to the transmission line shown in Fig. 12.5. The ratings and reactances of the machines and transformers are


Machines 1 and 2: 100 MVA, 20 kV;  $X''_d = X_1 = X_2 = 20\%$ ,

$X_0 = 4\%$ ,  $X_n = 5\%$

Transformers  $T_1$  and  $T_2$ : 100 MVA, 20/345 kV ;  $X = 8\%$




Both transformers are solidly grounded on two sides. On a chosen base of 100 MVA, 345 kV in the transmission-line circuit the line reactances are  $X_1 = X_2 = 15\%$  and  $X_0 = 50\%$ . The system is operating at nominal voltage without prefault currents when a bolted ( $Z_f = 0$ ) single line-to-ground fault occurs on phase A at bus ③. Using the bus impedance matrix for each of the three sequence networks, determine the subtransient current to ground at the fault, the line-to-ground voltages at the terminals of machine 2,

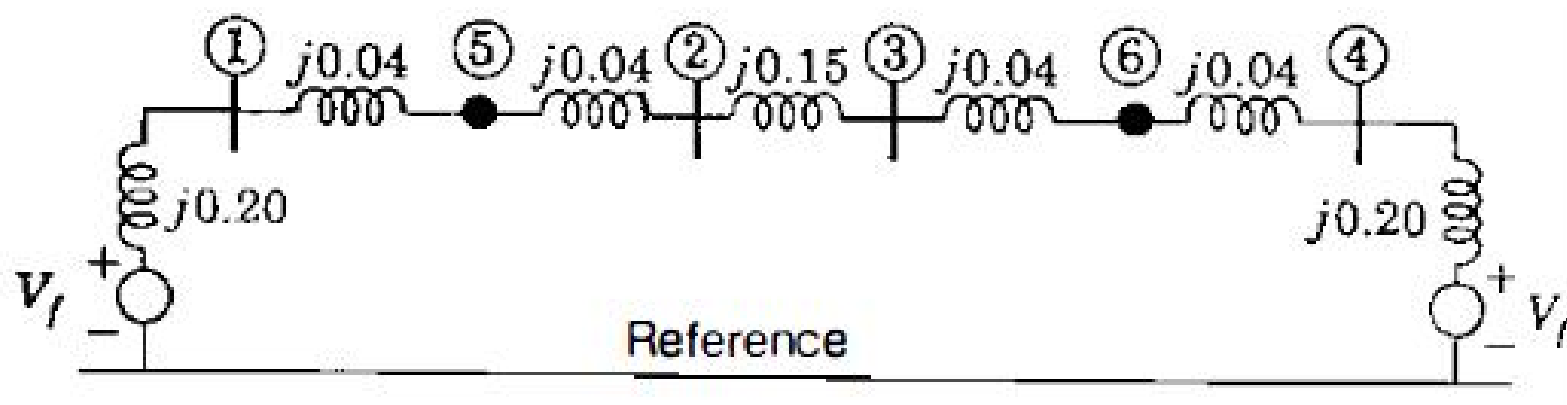

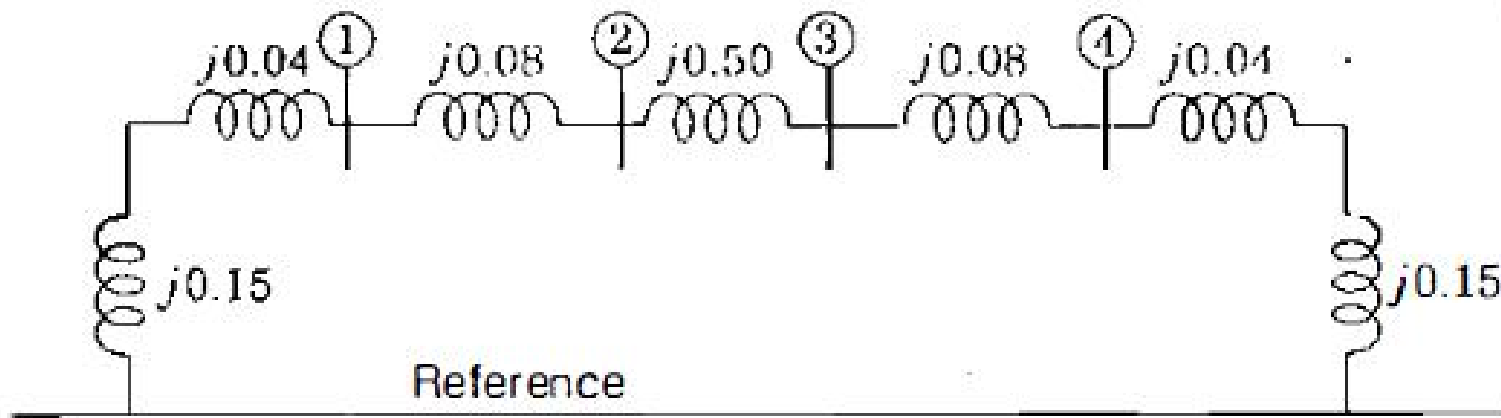
## Positive Sequence Network

$$Z(\text{positive sequence}) = Z(\text{negative sequence}) = j0.1696 \text{ p.u.}$$


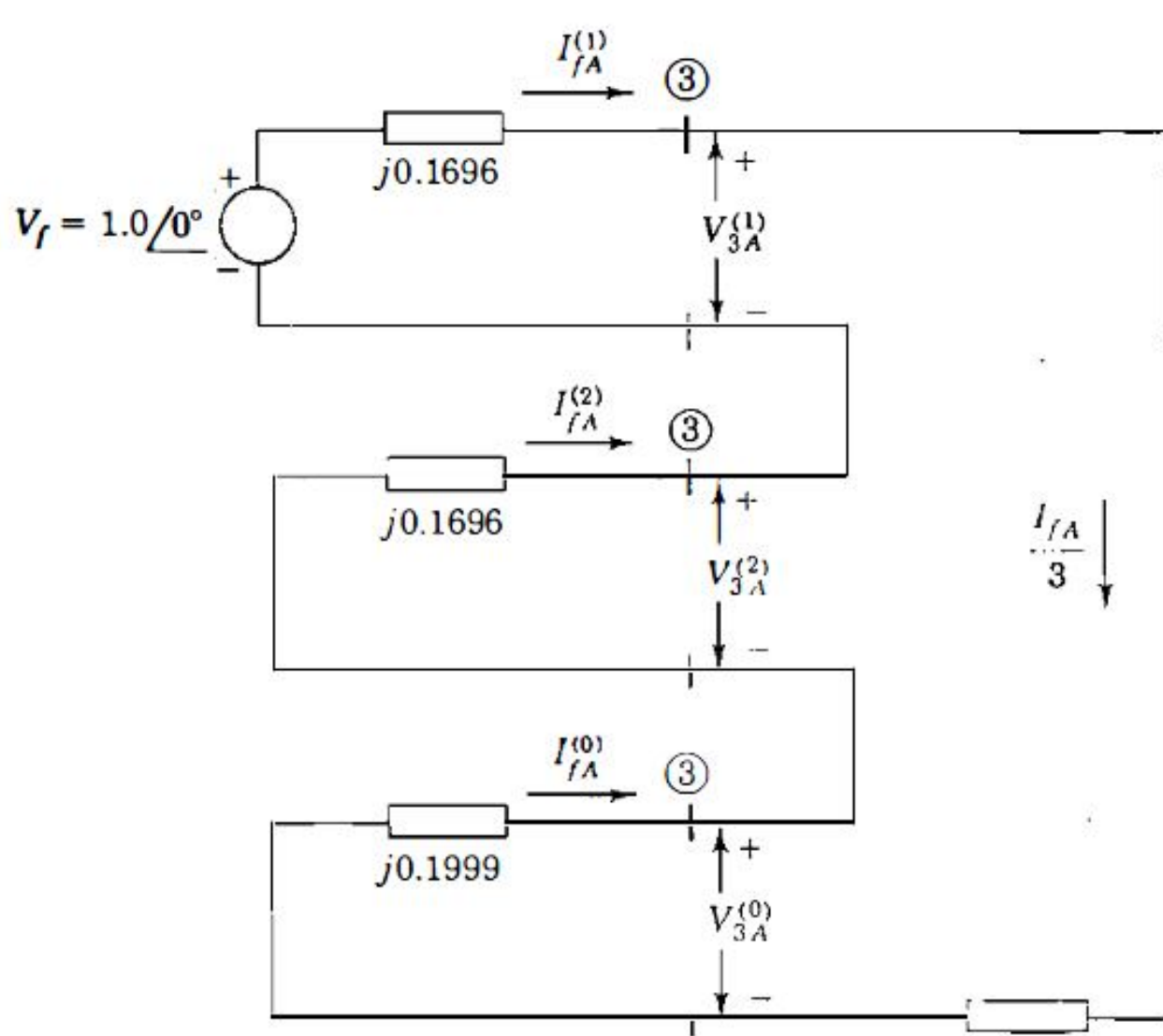
## Zero Sequence Network

$$Z(\text{zero sequence}) = j0.1999 \text{ p.u.}$$



$$\begin{aligned}
 I_{fA}^{(0)} = I_{fA}^{(1)} = I_{fA}^{(2)} &= \frac{V_f}{Z_{33}^{(1)} + Z_{33}^{(2)} + Z_{33}^{(0)}} \\
 &= \frac{1.0 \angle 90^\circ}{j(0.1696 + 0.1696 + 0.1999)} = -j1.8549 \text{ per unit}
 \end{aligned}$$



The total current in the fault is

$$I_{fA} = 3I_{fA}^{(0)} = -j5.5648 \text{ per unit}$$

and since the base current in the high-voltage transmission line is  $100,000 / \sqrt{3} \times 345 = 167.35 \text{ A}$ , we have

$$I_{fA} = -j5.5648 \times 167.35 = 931 \angle 270^\circ \text{ A}$$

Find the line to ground voltages at the terminals of machine 2

The terminals of machine 2 is Bus number 4

So we have to use the following equations

$$V_{4a}^{(0)} = -Z_{43}^{(0)} I_{jA}^{(0)}$$

$$V_{4a}^{(1)} = V_j - Z_{43}^{(1)} I_{jA}^{(1)}$$

$$V_{4a}^{(2)} = -Z_{43}^{(2)} I_{jA}^{(2)}$$

.

$$\mathbf{Z}_{bus}^{(1)} = \mathbf{Z}_{bus}^{(2)} = \begin{matrix} & \textcircled{1} & \textcircled{2} & \textcircled{3} & \textcircled{4} \\ \textcircled{1} & \left[ \begin{array}{cccc} j0.1437 & j0.1211 & j0.0789 & j0.0563 \\ j0.1211 & j0.1696 & j0.1104 & j0.0789 \\ j0.0789 & j0.1104 & j0.1696 & j0.1211 \\ j0.0563 & j0.0789 & j0.1211 & j0.1437 \end{array} \right] \end{matrix}$$

$$\mathbf{Z}_{\text{bus}}^{(0)} = \begin{array}{c} \textcircled{1} \\ \textcircled{2} \\ \textcircled{3} \\ \textcircled{4} \end{array} \begin{array}{c} \textcircled{1} \quad \textcircled{2} \quad \textcircled{3} \quad \textcircled{4} \\ \left[ \begin{array}{cccc} j0.1553 & j0.1407 & j0.0493 & j0.0347 \\ j0.1407 & j0.1999 & j0.0701 & j0.0493 \\ j0.0493 & j0.0701 & j0.1999 & j0.1407 \\ j0.0347 & j0.0493 & j0.1407 & j0.1553 \end{array} \right] \end{array}$$

$$V_{4a}^{(0)} = -Z_{43}^{(0)} I_{jA}^{(0)} = -(j0.1407)(-j1.8549) = -0.2610 \text{ per unit}$$

$$V_{4a}^{(1)} = V_f - Z_{43}^{(1)} I_{jA}^{(1)} = 1 - (j0.1211)(-j1.8549) = 0.7754 \text{ per unit}$$

$$V_{4a}^{(2)} = -Z_{43}^{(2)} I_{jA}^{(2)} = -(j0.1211)(-j1.8549) = -0.2246 \text{ per unit}$$

$$\begin{bmatrix} V_{4a} \\ V_{4b} \\ V_{4c} \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} -0.2610 \\ 0.7754 \\ -0.2246 \end{bmatrix} = \begin{bmatrix} 0.2898 + j0.0 \\ -0.5364 - j0.8660 \\ -0.5364 + j0.8660 \end{bmatrix} \\
 = \begin{bmatrix} 0.2898 \angle 0^\circ \\ 1.0187 \angle -121.8^\circ \\ 1.0187 \angle 121.8^\circ \end{bmatrix}$$

To express the line-to-ground voltages of machine 2 in kilovolts, we multiply by  $20/\sqrt{3}$ , which gives

$$V_{4a} = 3.346 \angle 0^\circ \text{ kV} \quad V_{4b} = 11.763 \angle -121.8^\circ \text{ kV} \quad V_{4c} = 11.763 \angle 121.8^\circ \text{ kV}$$