


Course title: Automated Industrial System

Course code: EE512

Sheet #4

Design the power, connections and control circuits using ladder diagram mentioning all the devices used for the following applications:

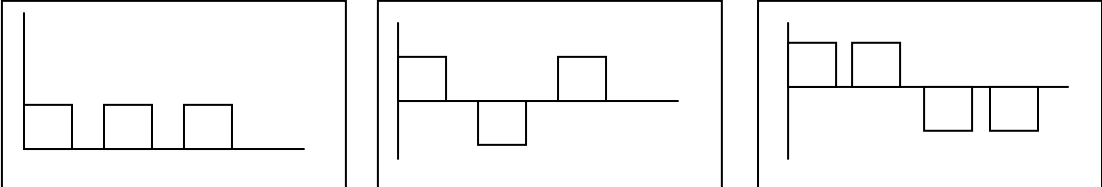- 1- A DC motor to be driven in one of the following ways according to user selection:



- 2- A motor operated in one of the following ways according to user selection:

